

BBM 203: Logic Design Lab

Fall 2020

Lab Experiment 5 – Report

Emirhan Topcu 21827899

Problem

Designing and simulating sequential circuits in Verilog HDL.

Convert the given state transition diagram to state transition table.

The image shows two handwritten state transition tables on graph paper. The first table is for DA and the second is for DB. Both tables have AB as the row header and xy as the column header.

Table 1: DA

AB \ xy	00	01	11	10
00	0	0	0	0
01	1	1	1	1
11	0	0	1	1
10	0	0	1	1

$DA = Ax + A'B$

Table 2: DB


AB \ xy	00	01	11	10
00	0	0	1	1
01	0	1	1	0
11	0	0	1	0
10	0	0	1	0

$DB = xy + A'B'x + A'By$

Determine the number of D flip flops you need to use to store the state information, and derive the input and output equations from the state transition table. Minimize the functions using K-Maps.

Present State		Inputs		Next State		Output	
A	B	X	Y	A	B	F ₁	F ₂
0	0	0	0	0	0	0	0
0	0	0	1	0	0	0	0
0	0	1	0	0	1	0	1
0	0	1	1	0	1	0	1
0	1	0	0	1	0	1	0
0	1	0	1	1	1	1	1
0	1	1	0	1	0	1	0
0	1	1	1	1	1	1	1
1	0	0	0	0	0	0	0
1	0	0	1	0	0	0	0
1	0	1	0	1	0	1	0
1	0	1	1	1	1	1	1
1	1	0	0	0	0	0	0
1	1	0	1	0	0	0	0
1	1	1	0	1	0	1	0
1	1	1	1	1	1	1	1

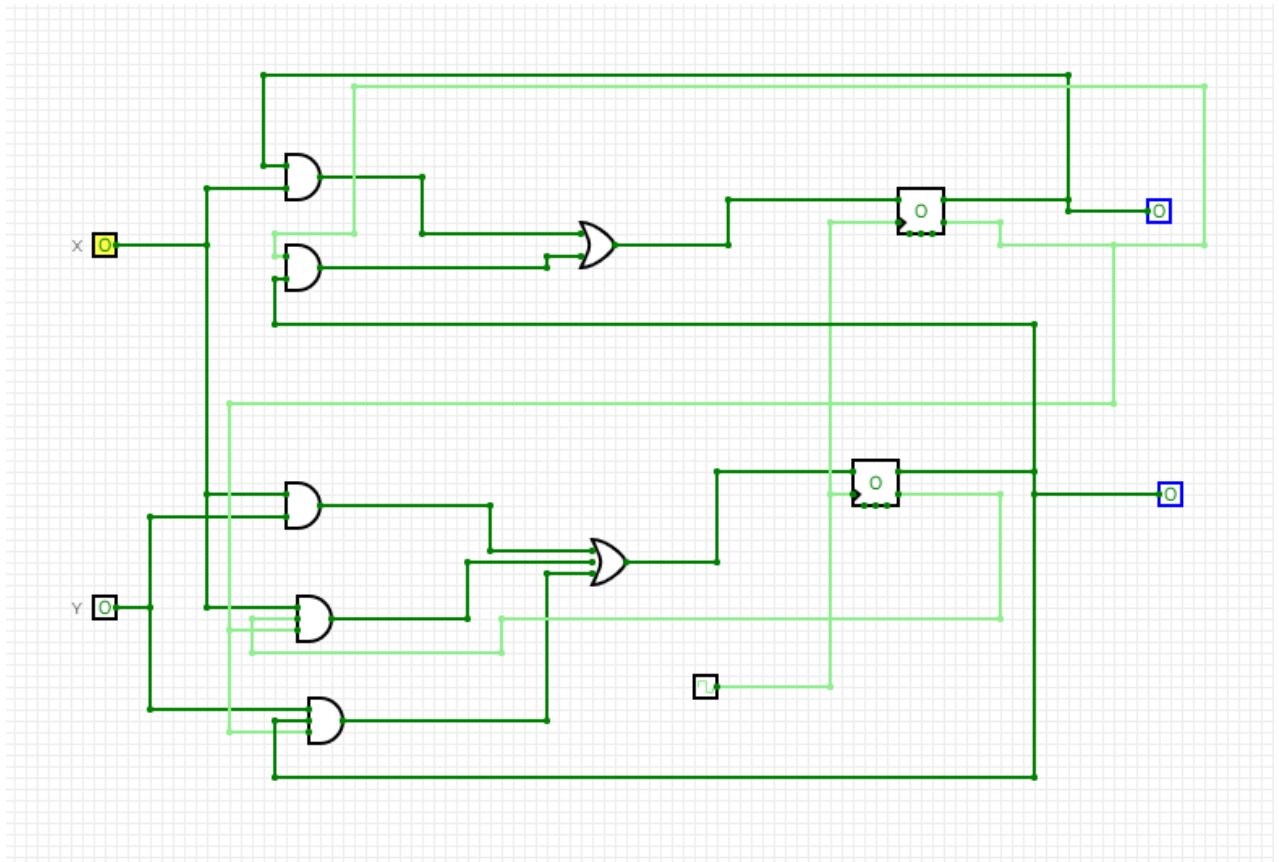Use the simplified functions to obtain the design schematic that uses D flip flops.



Include three Verilog code solutions for all specified modules:

Dflipflop.v

```
timescale 1ns / 1ps

module Dflipflop(
    input D,
    input clock,
    output reg Q
);

    always @ (posedge clock)
    begin
        Q <= D;
    end

endmodule
```

controller.v

```
`timescale 1ns / 1ps

`include "Dflipflop.v"

module controller(F, x, y, clock);

input x, y, clock;
output [1:0] F;
reg [1:0] p_state = 2'b00;
wire [1:0] n_state;

Dflipflop flipflop1(.D((~p_state[1] & ~p_state[0] & x) | (~p_state[1] & p_state[0] & y) | (x & y)), .clock(clock), .Q(n_state[0]));
Dflipflop flipflop2(.D((~p_state[1] & p_state[0] | (p_state[1] & x)), .clock(clock), .Q(n_state[1]));

always@ (posedge clock)
begin
    p_state <= n_state;
end

assign F [1] = n_state [1];
assign F [0] = n_state [0];

endmodule
```

controller_tb.v

```
`include "controller.v"

module controller_tb;

    reg x, y, clock = 0;
    wire [1:0] F;


    controller UUT(
        .x(x), .y(y), .clock(clock), .F(F)
    );

    always begin
        #5
        clock = 1;
        #5
        clock = 0;
    end

    initial begin
        x = 0; y = 0;
        #50 x = 1;
        #50 y = 1;
        #50 x = 1; y = 1;
        #50 x = 0;
        #50 x = 0;
        #50 x = 1;
        #50 y = 0;
        #50 x = 1; y = 0;
        #50 x = 0;
        #50 x = 1;
        #50 y = 0;
        #50 x = 1; y = 1;
        #50 x = 1; y = 0;
        $finish;
    end

end
```

 Include the obtained waveform and explain.



I've checked for all the inputs and it works as it supposed to. For all the edges in the state transition diagram, I included a test block in the test bench and every execution for every edge works perfectly.